

Lab 3.1 Report

Name: Joshua Dong

UT eID: jid295

Section: MW 11-12 AM

Problem No: 12.10.D

Submission CheckList

- Answer the [preparatory questions](#).
- Submit the cover sheet
- Karnaugh maps and simplification for each input of the D FlipFlop. [20] points
- Attach a screenshot of your SimUAid circuit
- The SimuAid circuit file